

Assignment 7

AI24BTECH11008- Sarvajith

14. For the circuit shown in the figure below, assume that diodes D_1, D_2 and D_3 are ideal. The DC components of voltages v_1 and v_2 respectively are

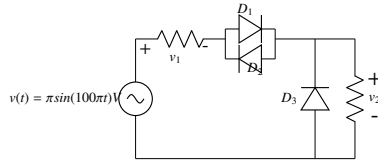


Fig. 0.1: 1

- (A) 0 V and 1 V
 (B) -0.5 V and 0.5 V
 (C) 0 V and 0.5 V
 (D) 1 V and 1 V
15. For the power semiconductor devices IGBT, MOSFET, Diode and thyristor, which one of the following statements are true?
- (A) All the four are majority carrier devices.
 (B) All the four are minority carrier devices.
 (C) IGBT and MOSFET are majority carrier devices, whereas Diode and Thyristor are minority carrier devices.
 (D) MOSFET is majority carrier device, whereas IGBT, Diode, Thyristor are minority carrier devices.
16. Consider $g(t) = \begin{cases} t - [t], & t \geq 0 \\ t - [t], & \text{otherwise} \end{cases}$ where $t \in \mathbb{R}$. Here $[t]$ represents the largest integer less than or equal to t and $\lceil t \rceil$ denotes the smallest integer greater than or equal to t . The coefficient of the second harmonic component of the Fourier series representing $g(t)$ is?
17. Let $I = c \iint_R xy^2 dx dy$, where R is the region shown in the figure and $c = 6 \times 10^{-4}$. The value of I is equal to? (Give the answer upto 2 decimal places.)

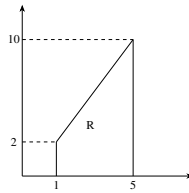


Fig. 0.2: 2

18. The power supplied by the 25V source in the figure shown below isW?

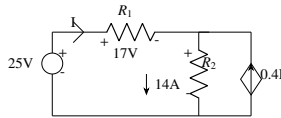


Fig. 0.3: 3

19. The equivalent resistance between the terminals A and B is Ω .

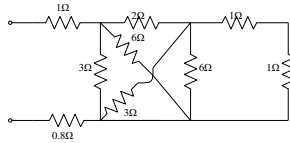


Fig. 0.4: 4

20. A three-phase, 50Hz, star connected cylindrical-rotor synchronous machine is running as a motor. The machine is operated from a 6.6kV grid and draws current at unity power factor (UPF). The synchronous reactance of the motor is 30Ω per phase. The load angle is 30° . The power delivered to the motor in kW is (Give the answer up to one decimal place).
21. A bus power system consists of four generator buses indexed as G1, G2, G3, G4 and six load buses indexed as L1, L2, L3, L4, L5 and L6. The generator-bus G1 is considered as slack bus, and the load buses L3 and L4 are voltage controlled buses. The generator at bus G2 cannot supply the required reactive power demand, and hence it is operating at its maximum reactive power limit. The number of non-linear equations required for solving the load flow problem using Newton-Raphson method in polar form is
22. Consider the unity feedback control system shown. The value of K that results in a phase margin of the system to be 30° (give the answer up to 2 decimal places.)
23. The following measurements are obtained on a single phase load: $V = 220V \pm 1\%$, $I = 5.0A \pm 1\%$ and $W = 555W \pm 2\%$. If the power factor is calculated using these measurements, the worst case error in the calculated power factor in percent

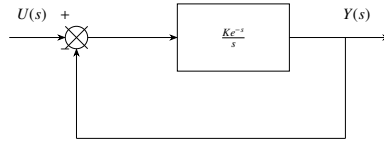


Fig. 0.5: 5

is(Give answer up to one decimal place.)

24. In the converter circuit shown below, the switches are controlled such that the load voltage $v_0(t)$ is a 400 Hz square wave. The RMS value of the fundamental component

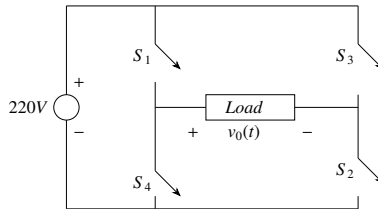


Fig. 0.6: 6

of $v_0(t)$ in volts is

25. A 3-phase voltage source inverter is supplied from a 600V DC source as shown in the figure below. For a star connected resistive load of 20Ω per phase, the load power for 120° device connection. in kW is

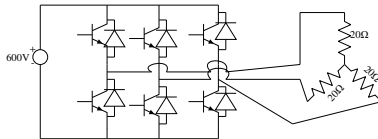


Fig. 0.7: 7

26. A function $f(x)$ is defined as $f(x) = \begin{cases} e^x, & x < 1 \\ \ln x + ax^2 + bx & x \geq 1 \end{cases}$ where $x \in R$. Which one of the following statements is TRUE?

- (A) $f(x)$ is NOT differentiable at $x = 1$ for any values of a and b .
- (B) $f(x)$ is differentiable at $x = 1$ for unique values of a and b .
- (C) $f(x)$ is differentiable at $x = 1$ for all values of a and b such that $a+b = e$.
- (D) $f(x)$ is differentiable at $x = 1$ for all values of a and b .